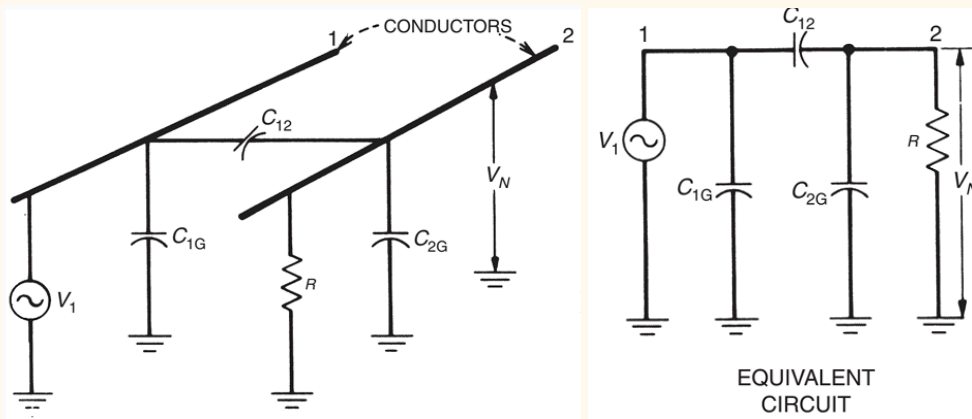


Capacitive Coupling




$$V_N = \frac{R \parallel \frac{1}{j\omega C_{2G}}}{\frac{1}{j\omega C_{12}} + \left(R \parallel \frac{1}{j\omega C_{2G}}\right)} V_1$$




$$V_N = \frac{j\omega C_{12} R}{1 + j\omega (C_{12} + C_{2G}) R} V_1$$

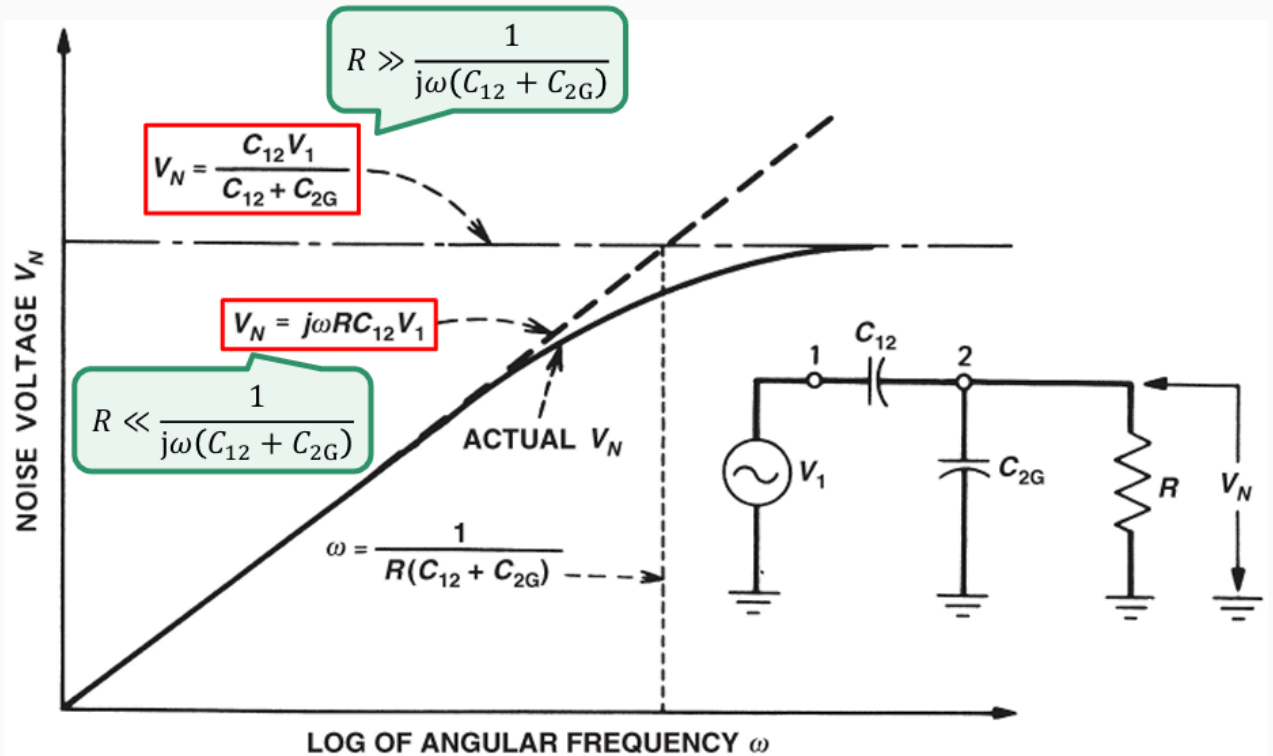V_N when $R \gg \frac{1}{\omega(C_{12} + C_{2G})}$ has a larger magnitude than V_N when $R \ll \frac{1}{\omega(C_{12} + C_{2G})}$.



Electric Field Shielding

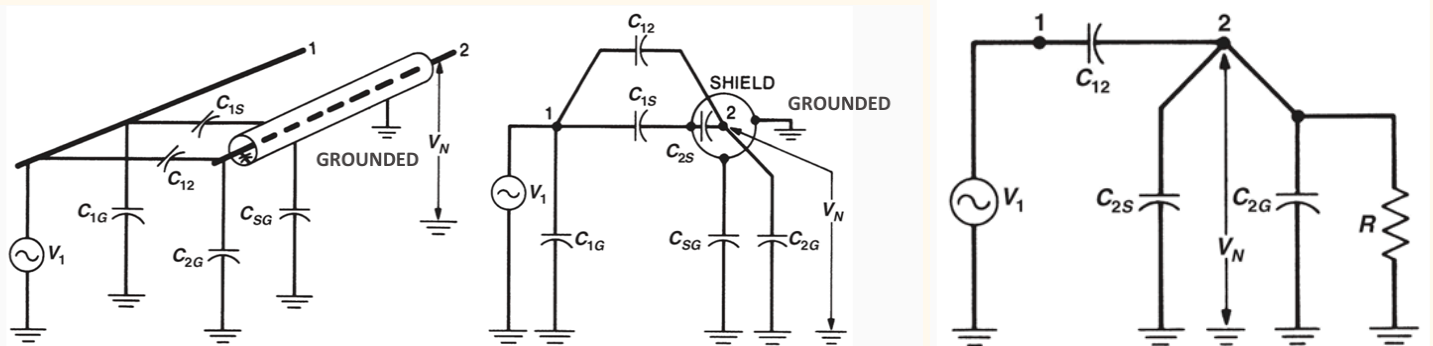

- Shield must be grounded. If conductor and shield are both floating $V_N = V_S$

When $R \ll \frac{1}{\omega(C_{12} + C_{2G} + C_{2S})}$:

$$V_N = \frac{j\omega C_{12}R}{1 + j\omega(C_{12} + C_{2G} + C_{2S})R} V_1$$



$$V_N = j\omega C_{12}R V_1$$


When $R \gg \frac{1}{\omega(C_{12} + C_{2G} + C_{2S})}$:

$$V_N = \frac{j\omega C_{12}R}{1 + j\omega(C_{12} + C_{2G} + C_{2S})R} V_1$$




$$V_N = \frac{C_{12}}{C_{12} + C_{2G} + C_{2S}} V_1$$


Inductive Coupling

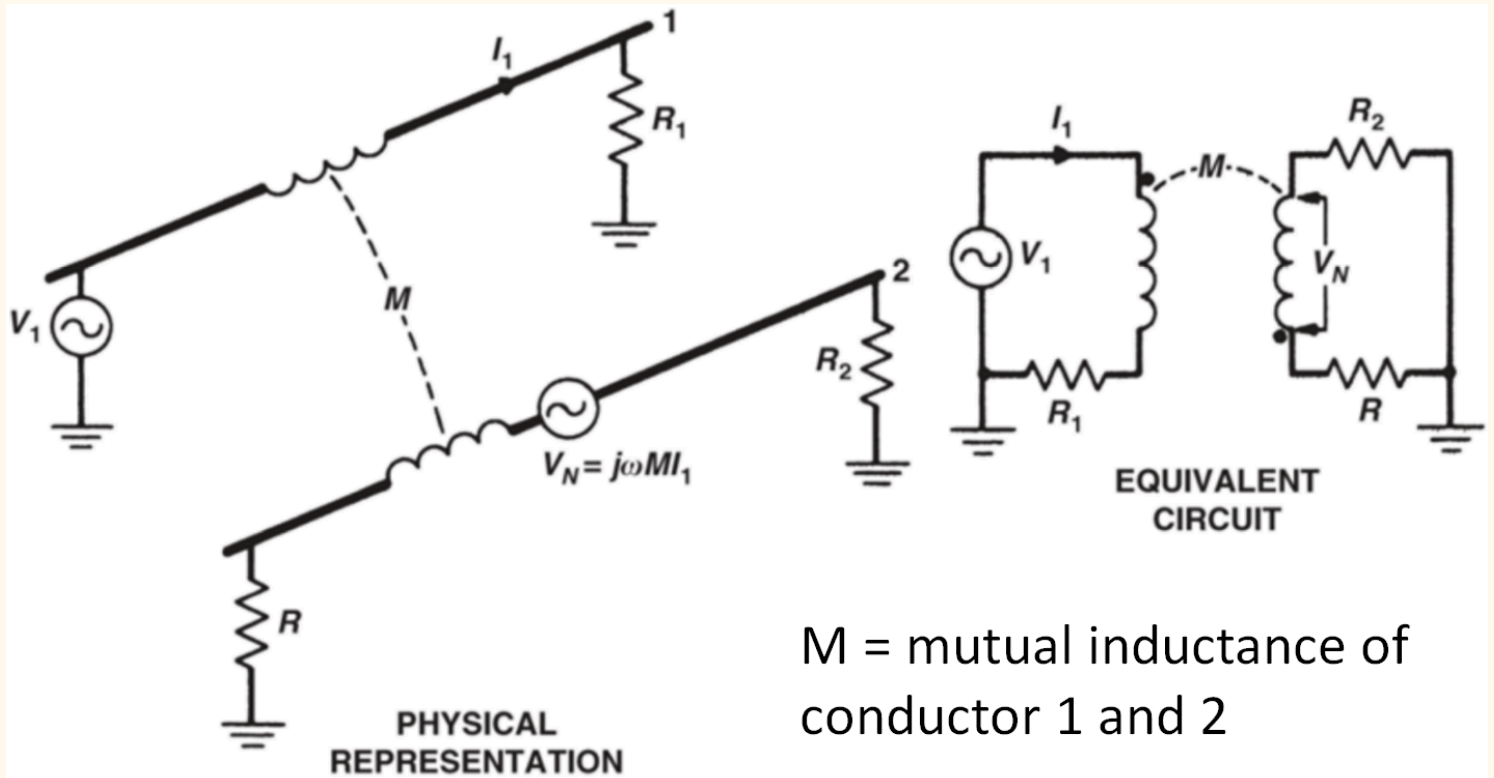

Magnetic Field Shielding

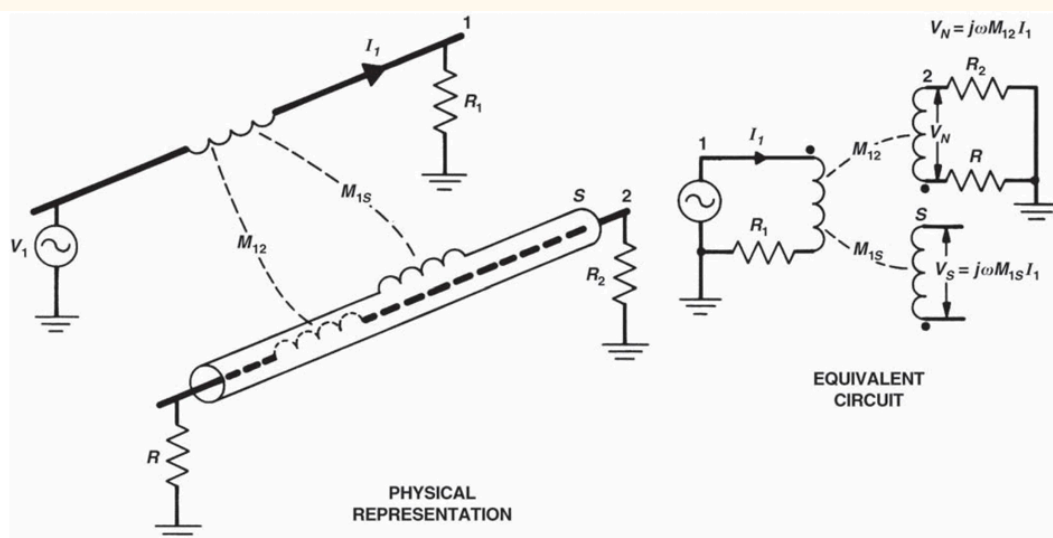

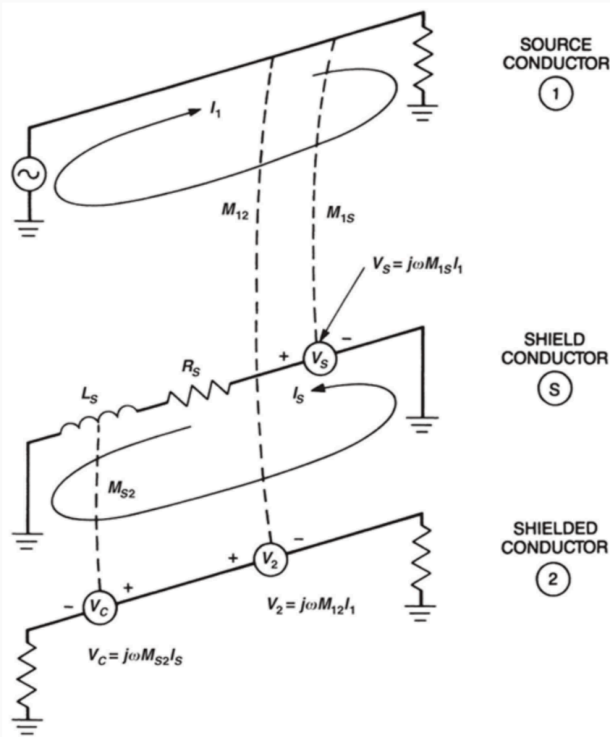- shield must be grounded at both ends for shield current to flow and act as shield



There are two voltage noises induced on conductor 2:

- V_2 is induced directly from conductor 1
- V_C is induced from the induced shield current

V_2 and V_C have different polarities, hence

$$V_N = V_2 - V_C$$

$$V_2 = j\omega M_{12} I_1$$

$$V_S = j\omega M_{1S} I_1$$

$$V_C = \frac{j\omega}{j\omega + \omega_c} V_S$$

$$M_{1S} = M_{12}$$

$$\omega_c = R_S / L_S$$

$$V_N = j\omega M_{12} I_1 \left(\frac{\omega_c}{j\omega + \omega_c} \right)$$

Low frequency
($\omega \ll \omega_c$)

High frequency
($\omega \gg \omega_c$)


$$V_N = j\omega M_{12} I_1$$

(Same as w/o shield)

$$V_N = M_{12} I_1 \omega_c$$

The shield does not help at low frequencies but limits the inductive noise at high frequencies.

32

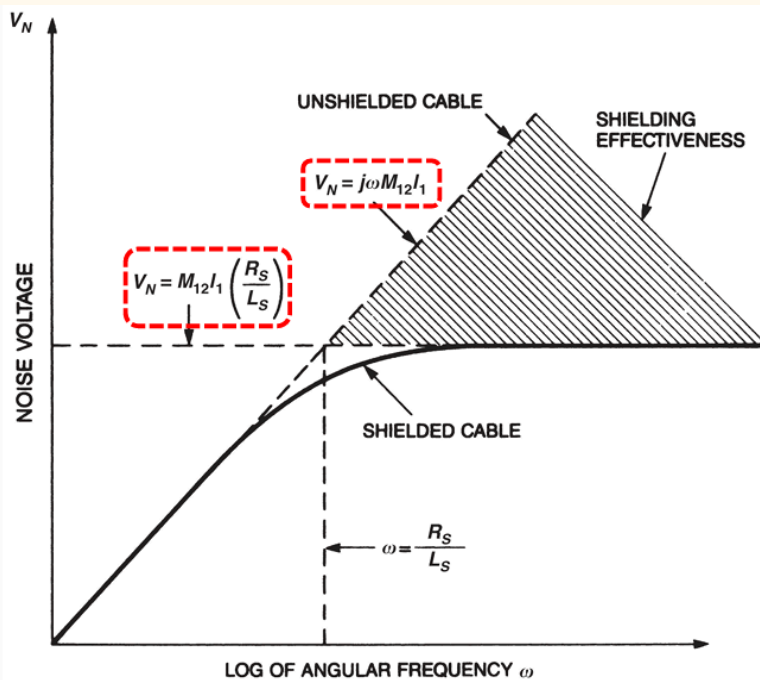

$$V_N = j\omega M_{12} I_1 \left(\frac{R_S / L_S}{j\omega + R_S / L_S} \right)$$

- ❑ To minimize pickup noise, one can reduce the shield resistance R_S .
- ❑ It is the induced shield current I_S that produces the magnetic field, which cancels a large percentage of the direct induction into conductor 2 from conductor 1.

In the ideal case, when the shield is short circuit, V_N is fully cancelled.

33