


white background for circuit and plots

UNITS in plot


EE3408C Project

- for IC design always starts from the current then the voltage is easy to find
 - then find the gm and what not
 - its possible to do voltage first also, but current as the reference is the way

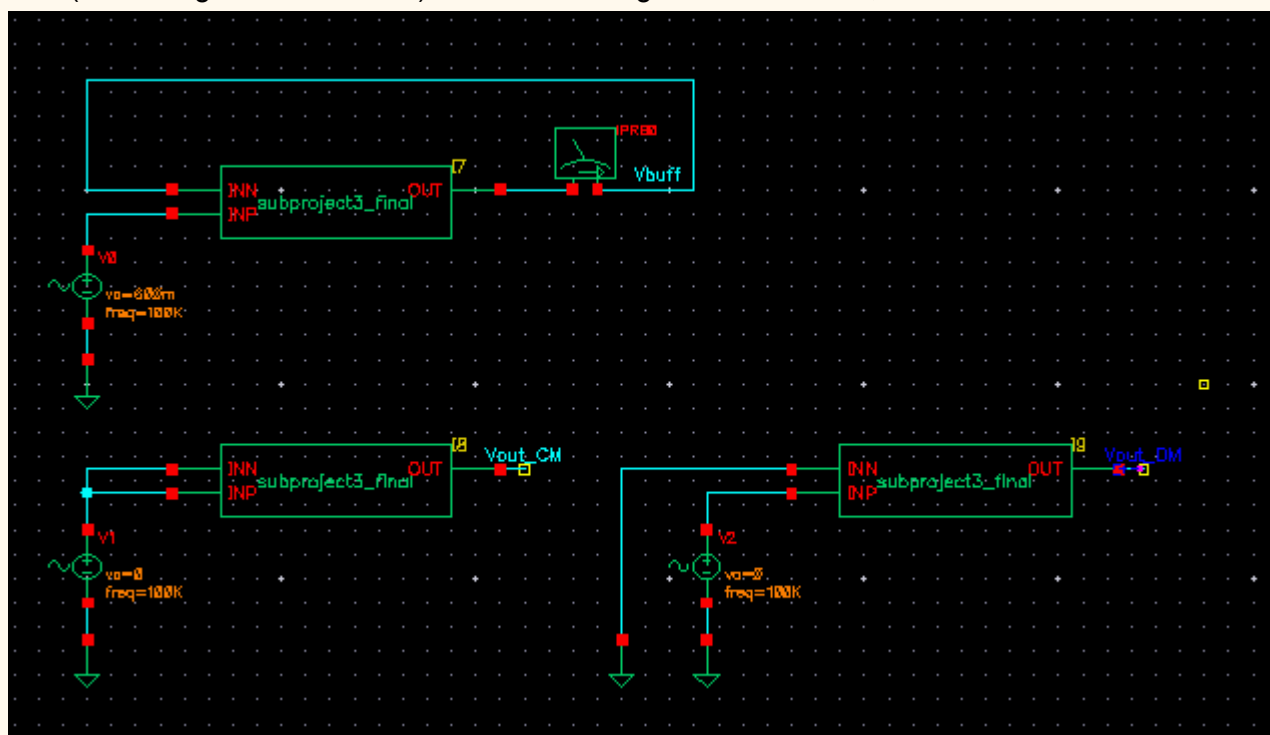STB (with unit gain buffer circuit) and AC should give the same PM, but it doesnt



Name	Vis	V1
Loop Gain Phase	☒	☒
Loop Gain dB20	☒	☒

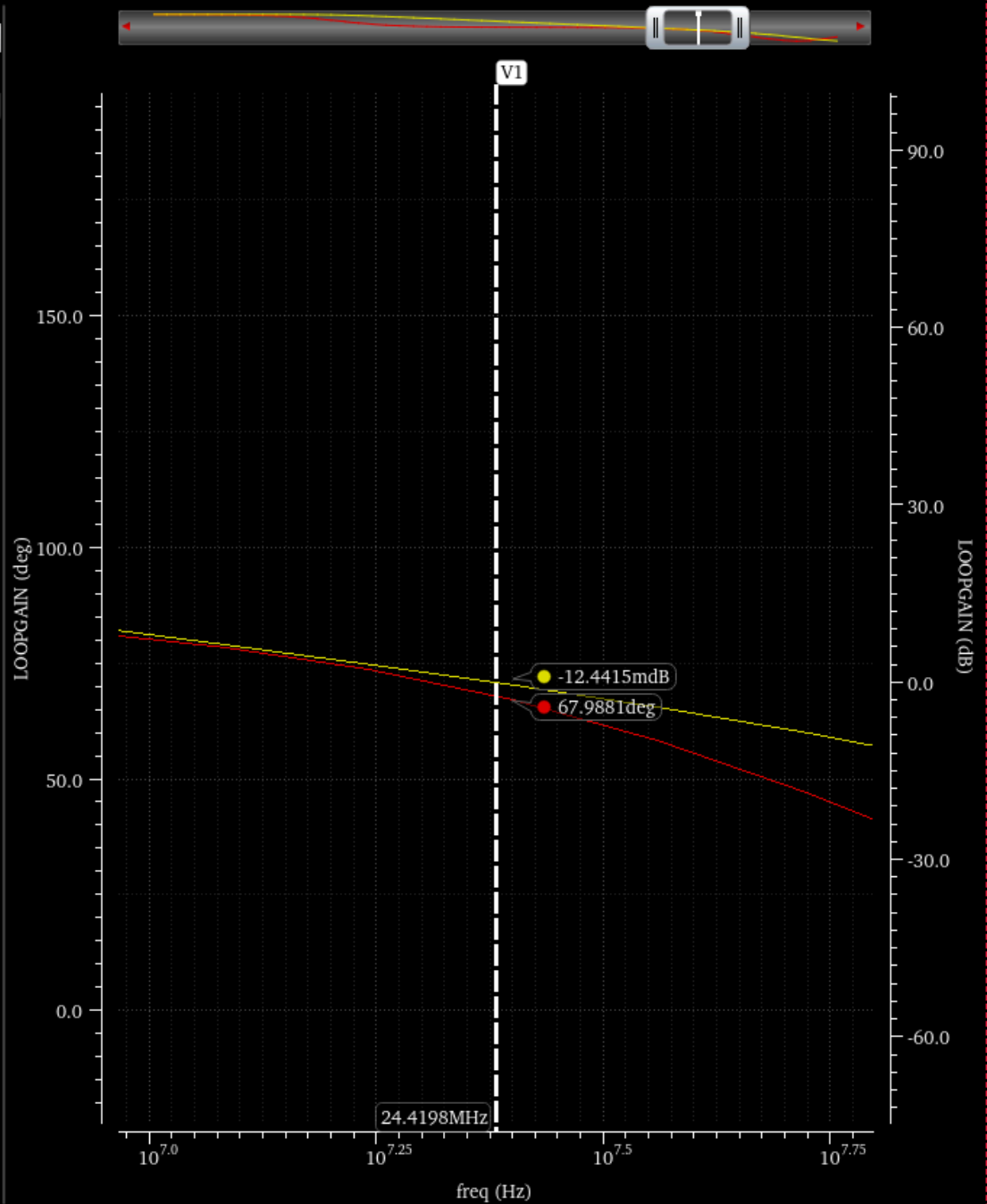


PM = 68 °


AC Response

Fri Nov 14 12:03:08 2025 2

Name	Vis	V1
v /Vout_CM; ac dB20(V)		-37.8267dB
v /Vout_DM; ac dB20(V)		-28.....5m dB
v /Vout_DM; ac deg(V)		-93.....5deg

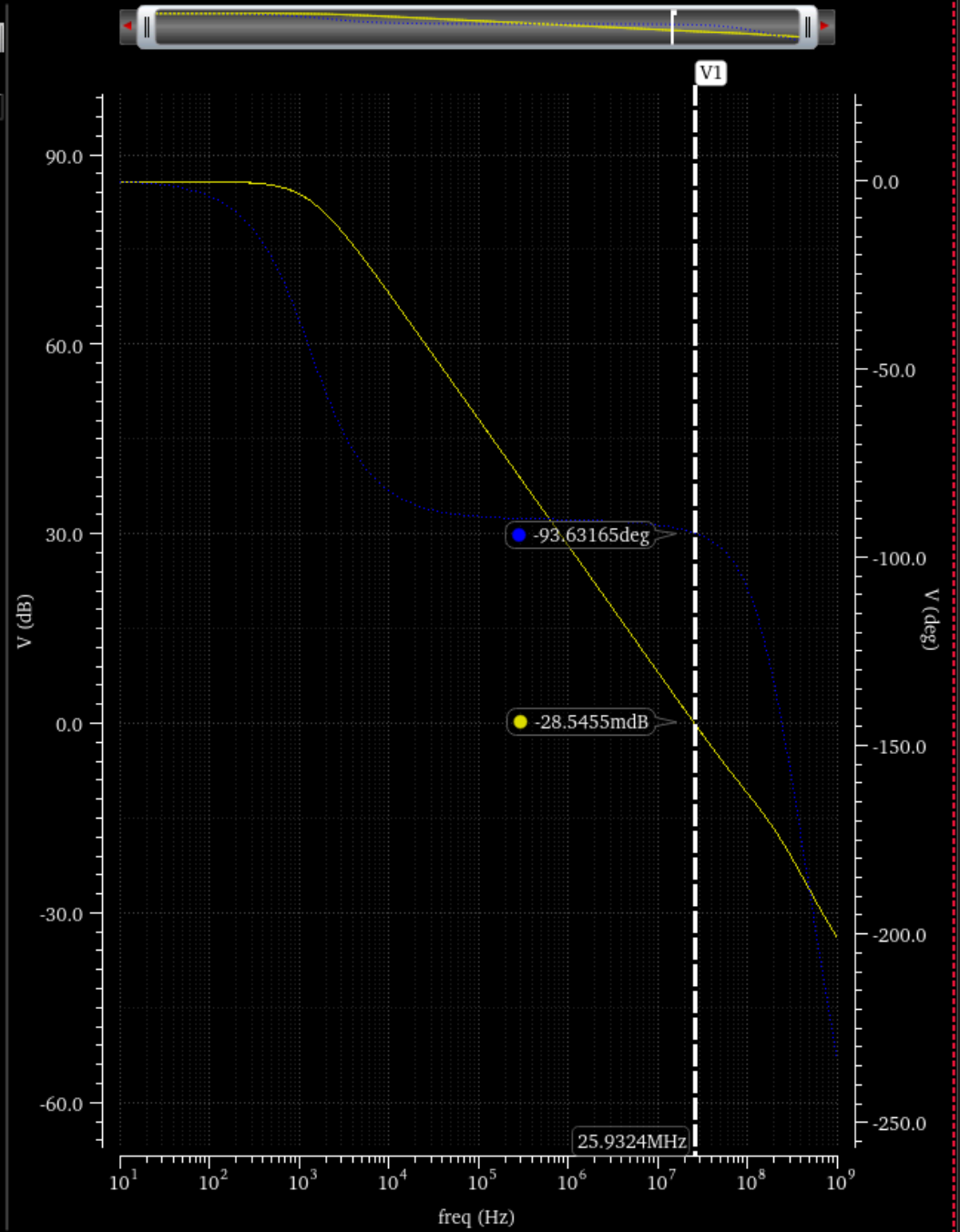

$$PM = -93.6 - -180 = 86.4^{\circ}$$

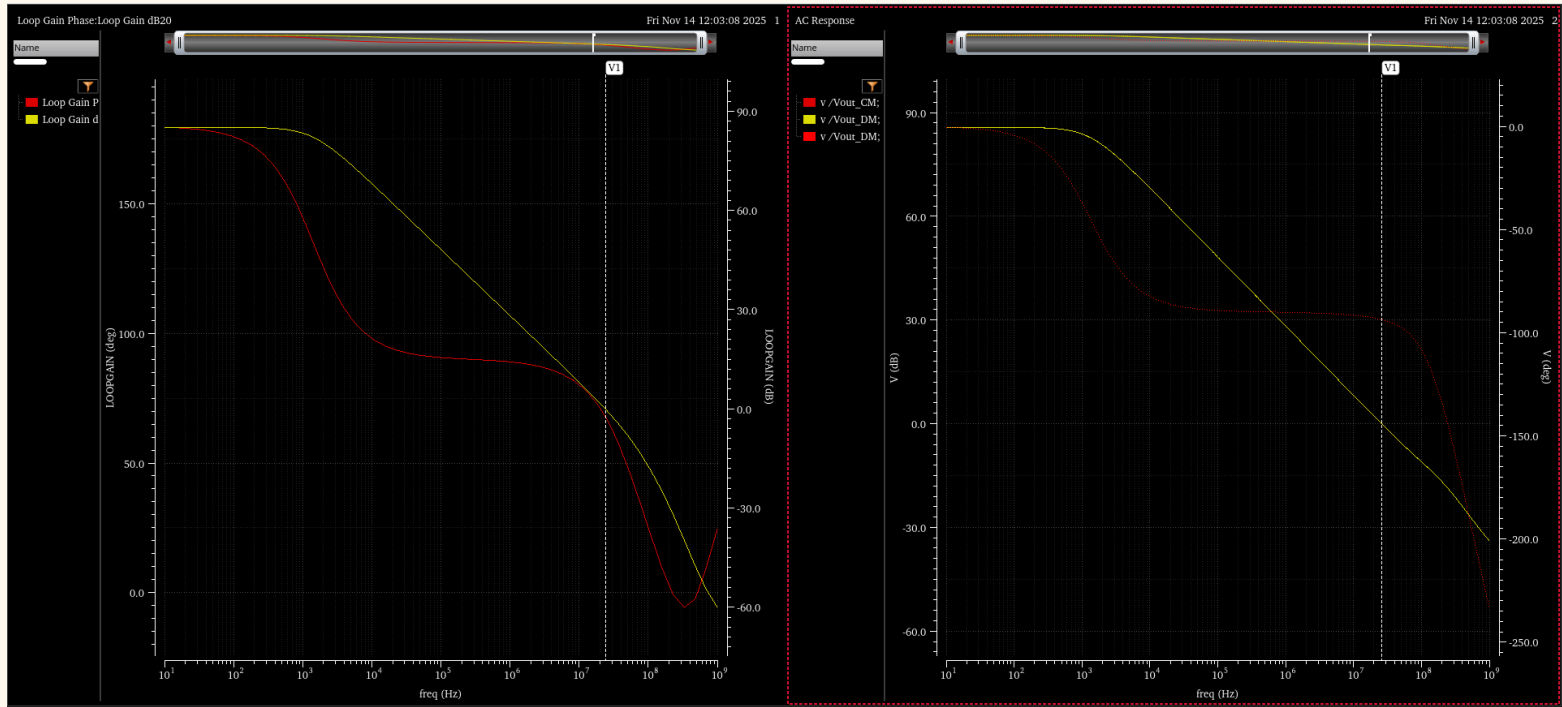

- prof dk need to wait for reply
- normally use STB, with the probe right at the inverting op amp input