

Q1. As shown in Fig. 1, NMOS transistor M_1 is part of a CS amplifier, and it operates in inversion region.

(1) Derive the expression of transistor intrinsic gain A_v , defined as $g_m r_o$, in terms of bias current I_D and the size W/L of M_1 .

(2) Explain why A_v cannot be increased by simply increasing I_D .

(10 Marks)

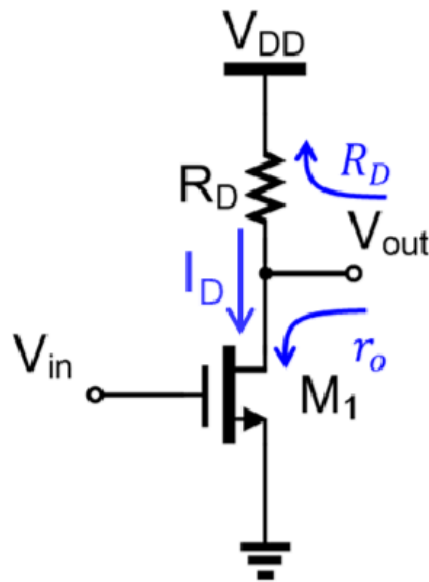
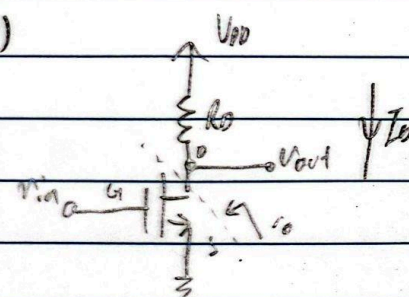


Fig. 1 CS amplifier with resistive load

1) 

i) $A_v = g_m r_o$ ← defined by question (even though should have -ve sign)

$$= 2 \sqrt{\frac{1}{2} \left(\frac{W}{L} \right) k_n' I_D} \times \frac{1}{2 I_D}$$

$$= \sqrt{2 \left(\frac{W}{L} \right) k_n' \frac{1}{I_D}} \times \frac{1}{2}$$

ii) increasing I_D , increases g_m in $\sqrt{I_D}$, but decreases r_o in $\frac{1}{I_D}$

$\therefore A_v$ cannot be increased by increasing I_D

Q2. Use small-signal model to derive the equivalent resistance r_{eq} looking to the transistor terminal as shown in Fig. 2 (a) and Fig. 2 (b) below. (20 Marks)

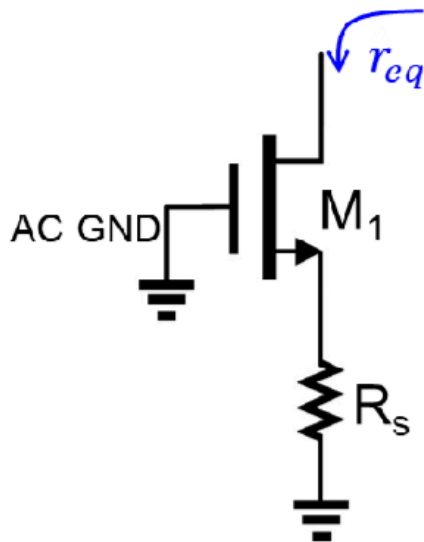


Fig. 2 (a)

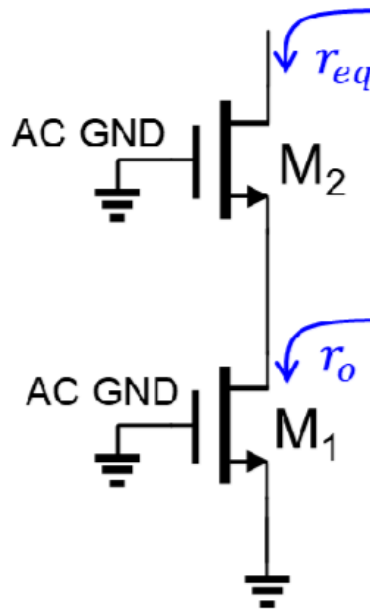
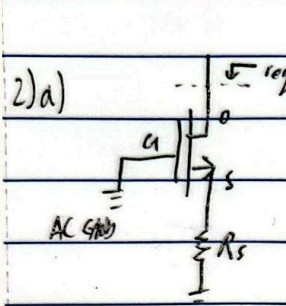


Fig. 2 (b)

2) a)  Assume in saturation
Assume body is grounded

$V_{gs} = V_{bs} = 0 - V_s = -V_s$

KCL at D: $i_o = g_m V_{gs} + g_{mb} V_{bs} + \frac{V_o - V_s}{r_o} = V_s / R_s$ $r_{eq} = \frac{\partial V_o}{\partial i_o}$

$i_o = -(g_m + g_{mb}) V_s + \frac{V_o - V_s}{r_o} = \frac{V_s}{R_s}$

$\downarrow \frac{\partial V_o}{\partial i_o}$


$\frac{\partial i_o}{\partial V_o} = -(g_m + g_{mb}) \frac{\partial V_s}{\partial V_o} + \frac{1}{r_o} - \frac{1}{r_o} \frac{\partial V_s}{\partial V_o} = \frac{\partial V_s}{\partial V_o} \frac{1}{R_s}$

$\frac{\partial V_s}{\partial V_o} = \frac{1}{r_o}$

$r_{eq} = \frac{\partial V_o}{\partial i_o} = R_s \times \frac{\partial V_o}{\partial V_s}$

$= R_s + r_o + R_s r_o (g_m + g_{mb})$

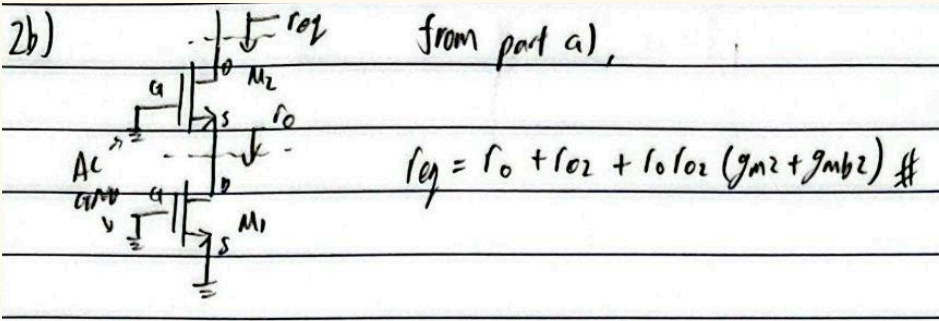$= \frac{R_s}{R_s + r_o + R_s r_o (g_m + g_{mb})}$



Q3. [Fig. 3](#) shows a common source amplifier with source degeneration resistor R_S . Derive the expression for amplifier voltage gain A_v . (20 Marks)


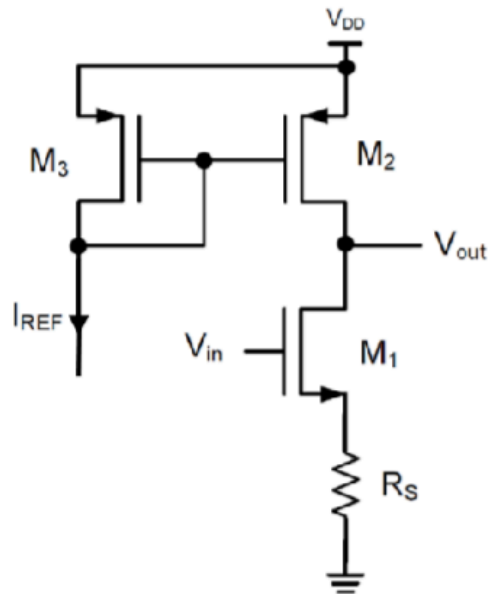


Fig. 3 CS amplifier with CSL and source degeneration resistor

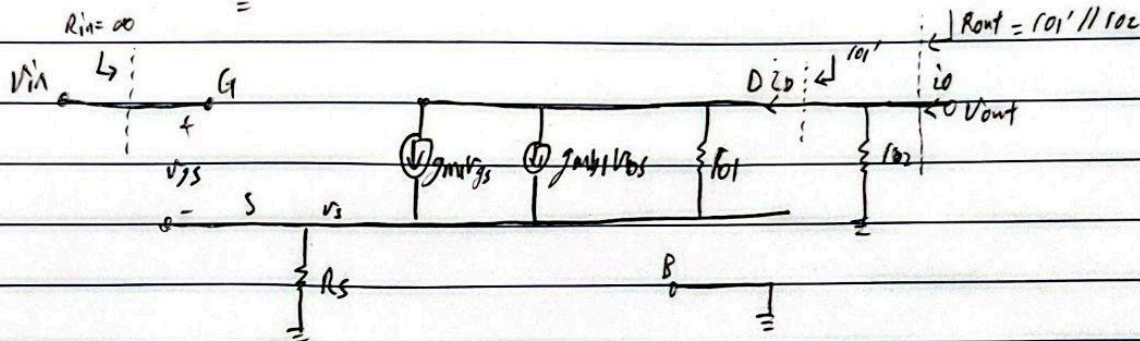

$$GM = \frac{d^2 \Delta}{d\alpha^2} \bigg|_{\alpha=0}$$

$$i_o = g_{m1} v_{gs} + g_{m2} v_{gs} + \frac{v_{out} - v_s}{r_{o1}} + \frac{v_{out}}{r_{o2}}$$

$$i_o = g_{m1}(v_{in} - v_s) + g_{mb1}(0 - v_s) + \frac{v_{out} - v_s}{r_{o1}} - \frac{v_{out}}{r_{o2}}$$

since $\gamma_{\text{min}} = 0$

$$\frac{\partial \Pi}{\partial v_{in}} = g_{M1} - g_{M1} \frac{\partial v_s}{\partial v_{in}} - g_{M1} \frac{\partial v_s}{\partial v_{in}} - \frac{1}{r_{o1}} \frac{\partial v_s}{\partial v_{in}} + 0 = \frac{\partial v_s}{\partial v_{in}} \frac{1}{r_s}$$

$$\frac{\partial v_s}{\partial v_{in}} = \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{R_S}}$$

$$\therefore G_m = \frac{r_o, g_m}{r_o R_s (g_m + g_{mb}) + r_o + R_s}$$

$$A_v = \frac{v_{out}}{v_{in}} = -G_m R_{out}$$

$$= \frac{-101 \text{ gms}}{101 R_s (\text{gms} + \text{gms}) + 101 + R_s} \times \frac{101' 102}{101' + 102}$$

$$= f_{01} g_{m1} \times \frac{f_{02}}{f_{01}' + f_{02}}$$

$$\frac{-I_{o1} I_{o2} g_{m1}}{R_s + I_{o1} + I_{o2} + R_s I_{o1} (g_{m1} + g_{mb1})} \quad \#$$