
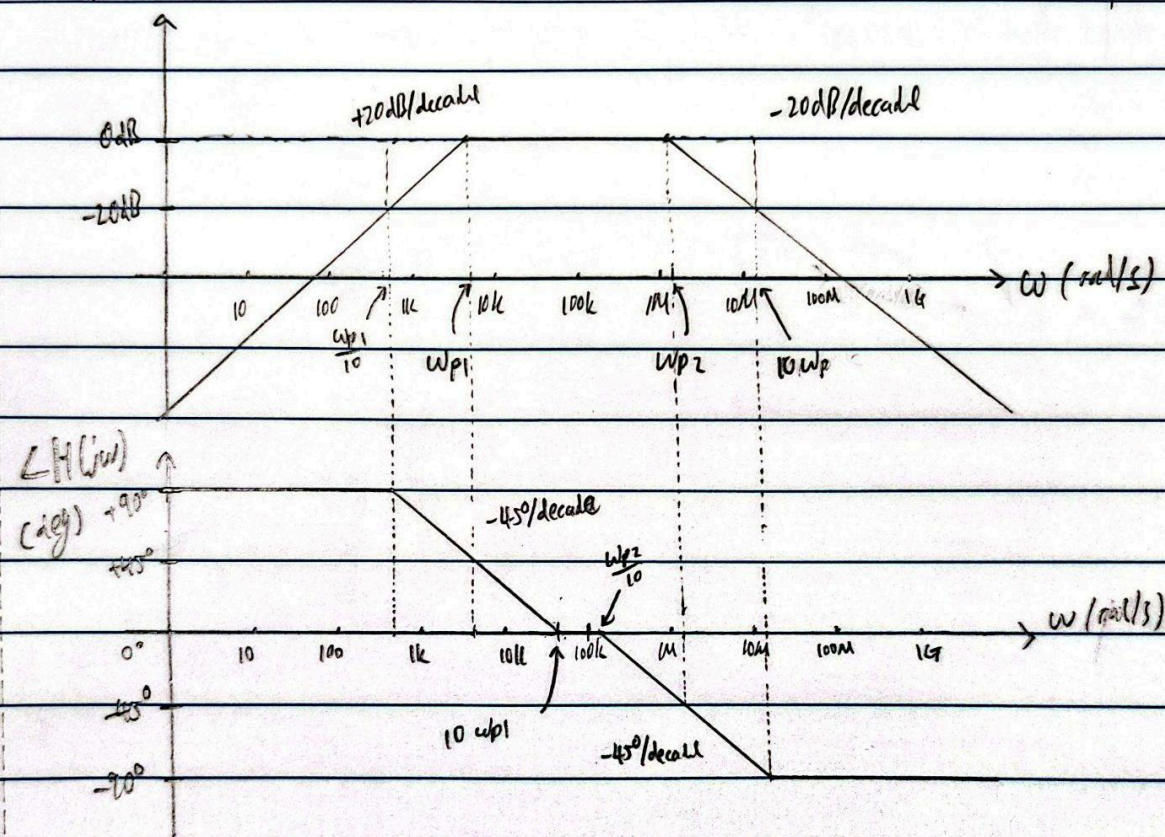


ii) $\omega_z = 0$ $\omega_{p1} = 20000/3$ $\omega_{p2} = 12500000/7$ $\Rightarrow f_z = 0 \text{ Hz}$ $f_{p1} \approx 1.061 \text{ kHz}$
 rad/s $\approx 6666.67 \text{ rad/s}$ $\approx 1785714.29 \text{ rad/s}$ $f_{p2} \approx 284.205 \text{ kHz}$

iii)	$ H(\omega) $	$ H(s) $	$s = j100k \approx 1$
------	---------------	----------	-----------------------

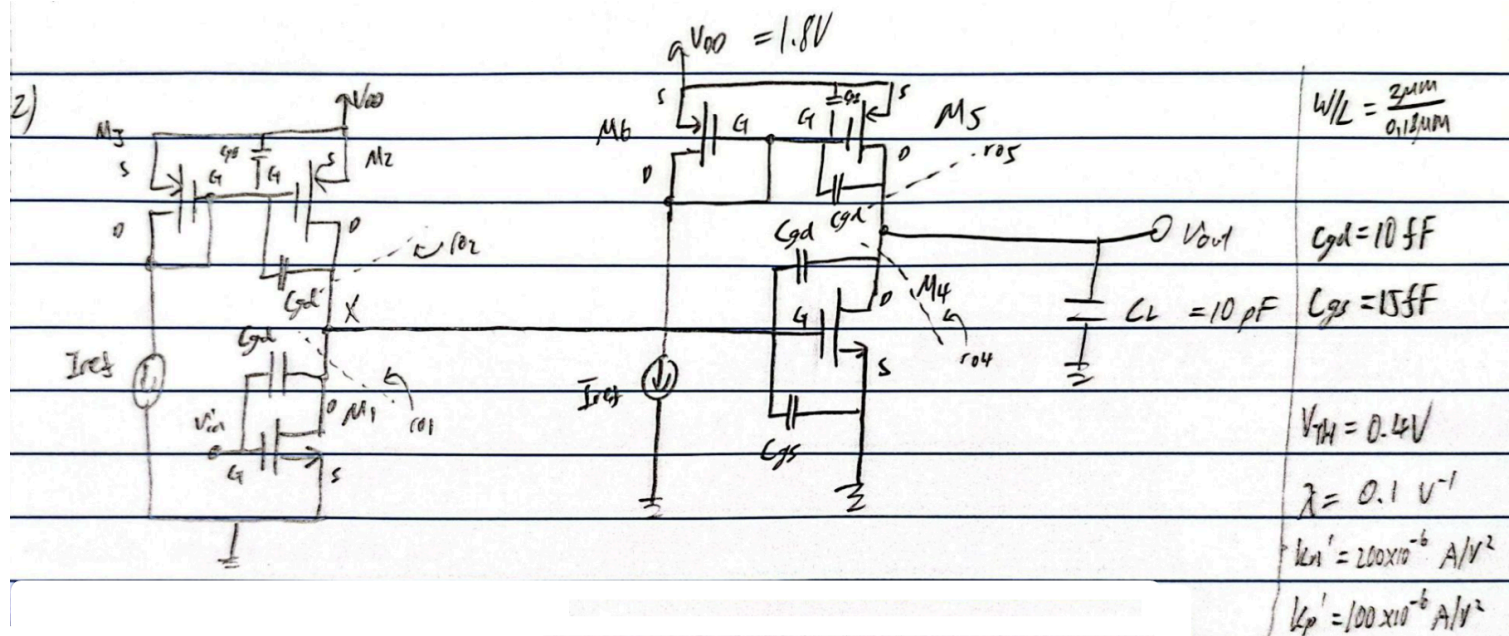

Question 2



i) $V_{out} = 0.9V$, $\lambda \neq 0 \Rightarrow$ cannot assume all $I_D = I_{ref}$ (there could be gain error)

$$\begin{aligned}
 M_4 \& M_5: \quad \frac{1}{2} k_p' \left(\frac{W}{L}\right)_5 (|V_{gs5}| - V_{TH})^2 (1 + \lambda_p |V_{ds5}|) &= \frac{1}{2} k_n' \left(\frac{W}{L}\right)_4 (V_{gs4} - V_{TH})^2 (1 + \lambda_n V_{ds4}) \\
 (|V_{gs5}| - 0.4)^2 (1 + 0.1 \times 0.9) &= 2 (V_x - 0.4)^2 (1 + 0.1 \times 0.9) \\
 (|V_{gs5}| - 0.4)^2 &= 2 (V_x - 0.4)^2
 \end{aligned}$$


$$\begin{aligned}
 M_6: \quad I_{D6} &= \frac{1}{2} k_p' \left(\frac{W}{L}\right)_6 (|V_{gs6}| - V_{TH})^2 (1 + \lambda_p |V_{ds6}|) \quad |V_{gs6}| = |V_{ds6}| \\
 10\mu &= \frac{1}{2} \times 100\mu \times \frac{2}{0.18} (\alpha - 0.4)^2 (1 + 0.1\alpha) \quad \text{let } |V_{gs6}| = \alpha \\
 0.018 &= (\alpha^2 - 0.8\alpha + 0.16) (1 + 0.1\alpha) \\
 0.018 &= \alpha^2 - 0.8\alpha + 0.16 + 0.1\alpha^3 - 0.08\alpha^2 + 0.016\alpha \\
 0.7\alpha^3 + 0.92\alpha^2 - 0.784\alpha + 0.142 &= 0 \\
 \alpha &= -9.998..., 0.5307..., 0.2676... \\
 -ve &\Rightarrow NA \quad < 0.4V = V_{TH} \Rightarrow NA
 \end{aligned}$$

$$\therefore |V_{gs6}| = |V_{ds6}| = 0.5307394994 V$$

$$\begin{aligned}
 \text{sub:} \quad 2(V_x - 0.4)^2 &= (0.5307394994 - 0.4)^2 \quad (|V_{gs5}| = |V_{ds6}|) \\
 V_x &= 0.4924467866 V \quad (\text{ignore negative solution of } \sqrt{\cdot})
 \end{aligned}$$

M1 & M2: from M2 & M1
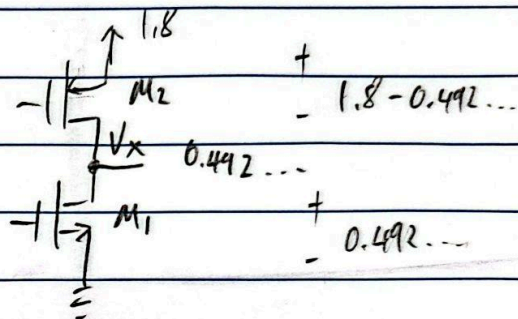
$$(V_{GS2} - 0.4)^2 = 2(V_{in} - 0.4)^2$$



M3 : from M2

$$|V_{GS2}| = |V_{GS1}| = 0.5307394994 \text{ V}$$

$$\Rightarrow |V_{GS2}| = 0.5307394994 \text{ V}$$

$$M_1 \& M_2 : \frac{1}{2} k_p' \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TH})^2 (1 + \lambda_p |V_{DS2}|) = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})^2 (1 + \lambda_n V_{DS1})$$

$$(|V_{GS2}| - 0.4)^2 (1 + 0.1 |V_{DS2}|) = 2 (V_{GS1} - 0.4)^2 (1 + 0.1 V_{DS1})$$

$$(0.5307394994 - 0.4)^2 (1 + 0.1 (1.8 - V_x)) = 2 (V_{in} - 0.4)^2 (1 + 0.1 V_x)$$

$$V_{in} = 0.4959704989 \text{ V} \quad (\text{ignoring -ve solution of } \sqrt{\cdot})$$

$$V_{in} \approx 0.496 \text{ V} \#$$

ii) current source load common source amplifier (Assume all body terminated is good for nmos & vop for pmos)

$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{o1} \parallel r_{o2}) \times -g_{m4} (r_{o4} \parallel r_{o5})$$

$$g_m = 2 \sqrt{\frac{1}{2} k_{np} \left(\frac{W}{L}\right) |I_D|}$$

$$= g_m^2 \times \left(\frac{r_o}{2}\right)^2$$

$$r_o = \frac{1}{\lambda |I_D|}$$


$$= 4 \left(\frac{1}{2} \times 200 \times 10^{-6} \times \frac{2}{0.18} \times 10 \mu\right) \times \frac{1}{4} \left(\frac{1}{0.1 \times 10 \mu}\right)^2$$

$$= 100000/V$$

↑ ignoring $\pi \Rightarrow$ all $I_D = I_{ref}$

$$\approx 11111.11 \text{ V/V} \#$$

$$\approx 81 \text{ dB} \#$$

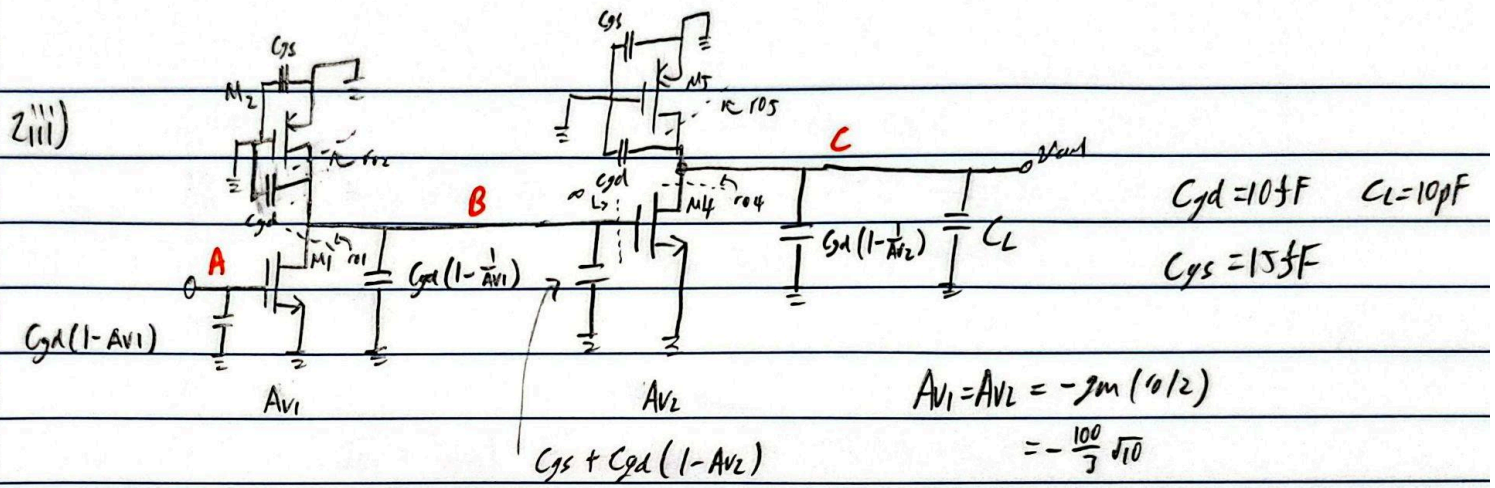

Association of poles w/ nodes :

at A: input driven with no $R_s \Rightarrow$ no poles

at B: $R = r_{o1} \parallel r_{o2}$ $C = C_{gd} + C_{gs}(1 - \frac{1}{A_{V1}}) + C_{gs} + C_{gd}(1 - A_{V2})$

$$\approx 500 \text{ k}\Omega \quad \approx 1099.19 \text{ fF}$$

$$\omega_{pe} = \frac{1}{RC} \approx 1819521.65 \text{ rad/s} \# \Rightarrow 289.59 \text{ kHz} \#$$


at C: $R = r_{o4} \parallel r_{o5}$ $C = C_{gd} + C_{gs}(1 - \frac{1}{A_{V2}}) + C_L$

$$\approx 500 \text{ k}\Omega \quad \approx C_L = 10 \text{ pF}$$

$$\omega_{pe} = \frac{1}{RC} \approx 200000 \text{ rad/s} \# \Rightarrow 31.83 \text{ kHz} \#$$

Question 3

3)

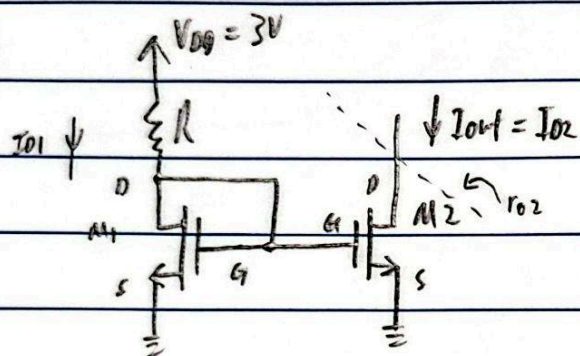

$V_{DS} = 0 \Rightarrow$ no body effect

$$L = 1 \mu\text{m}$$

$$k_n' = 200 \mu\text{A/V}^2$$

$$V_{TH} = 0.6 \text{ V}$$

$$\lambda = 0.02 \text{ V}^{-1}$$

a) $V_{DD} = 0.3 \text{ V}$

$$I_{D1} = 15 \mu\text{A}$$

$$I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$V_{GS1} - V_{TH} = 0.3$$

$$\frac{3 - 0.9}{R} = 15 \mu\text{A}$$

$$15 \mu\text{A} = \frac{1}{2} \times 200 \mu\text{A} \times \frac{W_1}{1 \mu\text{m}} \times 0.3^2 \times (1 + 0.02 \times 0.9)$$

$$V_{GS1} = 0.9 \text{ V}$$

$$R = 140 \text{ k}\Omega \#$$

$$W_1 = 2500/1527 \mu\text{m}$$

$$V_{DS1} = 0.9 \text{ V}$$

$$W_1 \approx 1.64 \mu\text{m} \#$$

b) Assume gain error free $V_{D2} = V_{D1}$


$$I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_{REF}$$

$$= \frac{W_2}{W_1} \times 15 \mu\text{A}$$


$I_{out}, \mu\text{A}$	7.5	30	45
$W_2, \mu\text{m}$	$0.5 W_1$	$2 W_1$	$3 W_1$
	≈ 0.82	≈ 3.28	$\approx 4.92 \#$

c) R_{out} of current source $= r_o = \frac{1}{\lambda I_{D1}}$

$R_{out}, \text{M}\Omega$	6.67	1.67	1.11
			$\#$

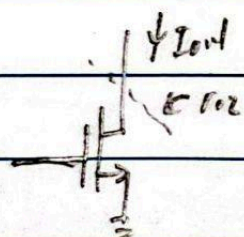

$\Rightarrow$

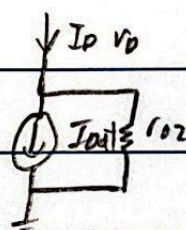

How I_D changes w/ $V_0 \Rightarrow \frac{\partial I_D}{\partial V_0} = \frac{\partial}{\partial V_0} \left(I_{out} + \frac{V_0}{r_{o2}} \right)$

$$= \frac{1}{r_{o2}} = \frac{1}{1.67 \text{ M}\Omega} \approx 0.6 \mu\text{A/V}$$

if V_0 is doubled from for example 1V to 2V,

I_{out} increased from $30 \mu\text{A} + 0.6 \mu\text{A}$ to $30 \mu\text{A} + 1.2 \mu\text{A}$

$\Rightarrow I_{out}$ changes $\approx 0.6 \mu\text{A}$ for every 1V in $V_0 \#$