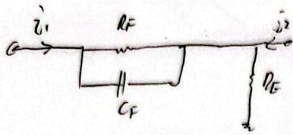


Derivation for Root Locus for Feedback-Zero Compensation



$$g_2 = \frac{v_2}{v_1} \Big|_{v_2=0} = f$$

$$= - \frac{R_E}{R_E + R_F \parallel \frac{1}{sC_F}}$$


$$= - \frac{R_E}{R_E + \frac{R_F}{1 + sR_F C_F}}$$

$$= - \frac{R_E + sR_E R_F C_F}{R_E + sR_E R_F C_F + R_F}$$


$$= - \frac{R_E}{R_F + R_E} \cdot \frac{1 + sR_F C_F}{1 + s \frac{R_E R_F C_F}{R_E + R_F}}$$

$$R_F \parallel \frac{1}{sC_F} = \frac{R_F \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}} = \frac{R_F}{1 + sR_F C_F}$$

$$g_h = \frac{v_1}{v_1} \Big|_{v_2=0}$$

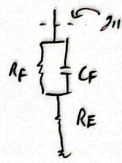

$$g_{22} = \frac{v_2}{v_2} \Big|_{v_1=0}$$

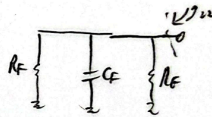

$$g_{21} = \frac{v_2}{v_1} \Big|_{v_2=0}$$

$\Rightarrow$ neglected

f has 1 zero & 1 pole

$$\omega_z = \frac{1}{R_F C_F} \quad \omega_p = \frac{R_E + R_F}{R_E} \cdot \frac{1}{R_F C_F}$$

$$\frac{1}{s+10} + \frac{1}{s+20} = \frac{1}{s+50}$$

$$(s+50)(s+20) + (s+10)(s+50) = (s+10)(s+20)$$

$$s^2 + 70s + 1000 + s^2 + 60s + 500 = s^2 + 30s + 200$$

$$s^2 + 100s + 1300 = 0$$

$$s = -15.4, -84.6$$