

Index

In this index individual filters, converters, etc. are entered by their initialism, i.e., BPF (bandpass filter).

A

- absolute value circuit, 583
- AC errors and parameters, 87, 324–326, 330
- AC excited transducers, 241
- AC integrator, 563
- AC loads, 316
- active filter design. *See also specific active filters*
 - all pass filters, 412–419
 - bandpass filters, 396–407
 - band rejection filters, 407–412
 - capacitor selection, 422–425
 - component values, 425
 - filter circuit biasing, 419–422
 - filter coefficient tables, 428–437
 - high pass filters, 388–395
 - introduction, 365–366
 - low pass filters, 376–388
 - op amp selection, 425–427
 - quality factor Q , 374–376
- AC to DC converter circuit, 585
- actuator, analog interface to
 - DAC, 524–529
- ADC (analog to digital converter)
 - analog interface from transducer, 231–236, 521–523
 - characterization, 247–248
 - comparator, 537
 - error budget, 236
 - interface circuit design

- ADC converter
 - characteristics, 263–264
- architectural decisions, 265–269
- input signal characteristics, 262–263
- introduction, 259
- op amp characteristics, 265
- power supply information, 260–261
- system information, 260
- selection criteria, 232
- ADC/transducer combinations, 231–236
- adders, 25–26
- AGC (automatic gain control) amplifier, 273
- AIA (analog interface amplifier), 244
- all pass filters, 365, 412–419, 436*t*
- analog ground, 484
- analog input drive circuits, high speed, 290–293
- antennas, 488–490
- antialiasing filters, 283–284
- application errors, common with
 - current feedback amplifier capacitor in the feedback loop, 544
 - shorted feedback resistor, 542–544
- current source, 541–542
- DC gain, 540–541

- decoupling capacitors, 549–550
- fully differential amplifier
 - incorrect common mode range, 548–549
 - incorrect DC operating point, 546–548
 - incorrect single ended termination, 544–546
- improper termination of unused sections, 538–540
- introduction, 533
- op amps
 - operated at less than unity gain, 533–535
 - used as a comparator, 535–538
- attenuation circuit, 574–576
- augmented differentiator, 566
- augmenting integrator, 564
- avalanche noise, 173–174, 176

B

- Balkenberg, M. E., 80
- band rejection filters, 76, 365, 407–412, 450
- bandwidth
 - decreased, 129
 - VFAs vs. CFAs, 140–143
- bandwidth parameters
 - for 0.1 dB flatness, 227
- BW, 197
- maximum output swing, 196–197

- bandwidth parameters
(*Continued*)
unity gain, 196
Bessel high pass filter, 394–395
Bessel low pass filter, 372–373,
403*t*, 428–437
biquad filter, 161
bits, 232
Black, Harry, 1
block diagrams
math and manipulations,
68–72
reduction rules, 72
transforms, 71*f*, 72
blocks, defined, 68*f*
Bode, H. W., 2, 74
Bode analysis, feedback circuits,
74–80
BPF (bandpass filter), 272, 276,
365, 374, 578–579
BPF (bandpass filter) design,
396–407
for high speed, 454–463
narrow (single frequency),
443–446
wide, 446–447
break point, 31
bricks, 3, 4
broadband noise parameter,
222–223
brown noise, 176
bubba oscillator, 359–360,
572–573
buffer amplifiers, 24, 282,
335–340
buffered phase shift oscillator,
357–358, 571–572
burst noise, 173
Butterworth bandpass filter,
404–407
Butterworth low pass filter, 371,
403*t*, 428–437
- C**
canonical equations, 89–91
canonical feedback loop, 72, 72*f*
capacitance
common mode input
parameter, 198
compensating for DAC,
334–335
differential input parameter,
198
input parameter, 197–198
load parameter, 198–199
capacitors, 31–32, 134–135,
422–425, 485, 491–493,
544
case temperature for 60 seconds,
228
ceramic resonator oscillator, 344
CFA (current feedback amplifier)
about, 121
application mistakes,
542–544
capacitor in the feedback loop,
544
factors influencing choice of,
281
inverting, 126–127
model, 121–122
newer, using, 341
noninverting, 124–125
shorted feedback resistor,
542–544
VFA vs., 97, 121, 127, 152
CFA (current feedback amplifier)
analysis
compensation of C_F and C_G ,
135–136
feedback resistor selection,
130–133
introduction, 121
stability analysis, 127–130
stability equation, 122–124
summary, 136
circuit analysis, 38–42
circuit design, 7, 249–256.
See also ADC: interface
circuit design; low voltage
amplifier circuit design
circuit noise model, 179
circuits. *See also specific circuits*
adders, 25–26
components of, 1
current source, 541–542
defined, 7
surface mount, 503
unstable, 341
circuit theory, 7
CMRR (common mode rejection
ratio), 87, 199–200
coarse transducers, 241
colors, noise, 174–176
common mode error, 548–549
common mode input voltage
condition, 218
common mode input voltage
range parameter, 218–219
common mode range, 513–518
common mode signal, 27
common mode voltage, 36
communication systems.
See wireless
communication systems
comparator, op amp used as,
535–538
compensated attenuator, 113–115
compensation. *See also* voltage
feedback compensation
compensation
of C_F and C_G , 135–136
dominant pole, 105–108
compensation
dominant pole, 118
gain, 108–109, 118
lead, 110–113, 118
lead/lag, 116–117, 119
Miller effect, 98
computers, analog, 2
conducted noise, 478, 499
constant current generator circuit,
580
continuous total dissipation
parameter, 228
control system terms, defined, 69
converter noise, 278
crosstalk parameter, 225

crystal oscillators, 341
 crystal resonator oscillators, 344
 current booster, 336–337
 current divider rule, 10–11
 current excited circuit, 237
 current parameters
 input bias current, 201–202
 input current range, 201
 input noise current, 202–203
 input offset current, 192–193, 202
 output current, 203
 low level condition, 203
 short circuit, 203
 short circuit current duration, 228
 supply current, 201
 shutdown, 201
 current source circuit, 541–542
 curve fitting filters, 588–591

D

DAC. *See also under* wireless communication systems
 to actuator interface, 235
 defined, 315
 dynamic range, 509
 interface circuit design, 524–529
 interfacing to loads
 AC errors and parameters, 330–334
 compensating for DAC capacitance, 334–335
 DC errors and parameters, 326–328
 error budget, 321–326
 increasing buffer amplifier current and voltage, 335–340
 introduction, 315
 load characteristics, 316
 selection criteria, 315
 types of, 316
 damping ratio, 97

data sheet parameters. *See also specific parameters*
 bandwidth
 for 0.1 dB flatness, 227
 BW, 197
 maximum output swing, 196–197
 unity gain, 196
 capacitance
 common mode input capacitance, 198
 differential input capacitance, 198
 input capacitance, 197–198
 load capacitance, 198–199
 common mode rejection ratio (CMRR), 199–200
 crosstalk, 225
 current
 input bias current, 201–202
 input current range, 201
 input noise current, 202–203
 input offset current, 192–193, 202
 output current, 203
 short circuit current duration, 228
 supply current, 201
 dissipation, 228
 error
 differential gain error, 193
 differential phase error, 227
 frequency condition, 200
 gain
 large signal voltage amplification gain condition, 195
 open loop voltage gain, 194–195
 gain bandwidth, 196, 200
 gain error, 193
 gain margin, 193–194
 harmonic distortion
 total, 213
 total plus noise, 213–215
 impedance, 225–226

input bias current, 201–202
 input offset voltage, 220–221
 introduction, 189–192
 noise
 broadband noise, 222–223
 equivalent input noise voltage, 222
 harmonic distortion, total, 213
 harmonic distortion, total + noise, 213–215
 input noise current, 202–203
 total harmonic distortion plus noise, 213–215
 null resistance condition, 210
 open loop
 transimpedance, 227
 transresistance, 210
 voltage gain, 194–195
 phase margin, 227
 power dissipation, 204
 power supply rejection ratio, 204–205
 resistance
 input resistance, 208–209
 input resistance differential, 209
 load resistance condition, 209
 output resistance, 210
 shutdown
 turn off time, 213
 turn off voltage parameter, 220
 turn on time, 213
 turn on voltage, 220
 signal source condition, 210
 slew rate, 210–212
 supply rejection ratio, 204
 temperature
 case temperature for 60 seconds, 228
 coefficient of input offset voltage, 193
 coefficient of the input offset current, 192–193

- data sheet parameters
 - (*Continued*)
 - lead temperature for 10 or 60 seconds, 229
 - maximum junction temperature, 216
 - operating free air temperature condition, 212–213
 - storage temperature, 217
 - thermal resistance
 - junction to ambient, 205–207
 - junction to case, 207–208
 - time
 - fall time, 213
 - rise time, 216
 - settling time, 216–217
 - turn off/turn on, 213
 - voltage
 - amplification gain
 - condition, 195
 - common mode input voltage condition, 218
 - common mode input voltage range, 218–219
 - differential input, 219
 - differential input voltage range, 219–220
 - differential large signal voltage amplification, 195–196
 - equivalent input noise voltage, 222
 - high level output voltage, 223
 - input offset voltage, 220–221
 - input offset voltage long term drift, 229
 - input voltage, 220
 - input voltage condition, 220
 - input voltage condition, common mode, 218
 - input voltage range condition, 218
 - input voltage range
 - condition or parameter, 218
 - large signal voltage amplification gain condition, 195
 - low level output voltage, 223
 - open loop voltage gain, 194–195
 - output voltage swing, maximum peak to peak, 223–224
 - output voltage swing, peak to peak, 225
 - step voltage peak to peak condition, 225
 - supply voltage condition, 217–218
 - supply voltage sensitivity, 199
 - turn off/turn on, 220
 - DC application error budget, 322–323
 - DC biasing techniques, 419–427
 - DC errors and parameters, 87, 326–328
 - DC gain, 540–541
 - DC loads, 316
 - DC offsets, 339–340
 - DC operating point, 546–548
 - decoupling capacitors, 44, 549–550
 - decoupling PCB, 495–498
 - Deliyannis filter, 455–457
 - differential amplifier, 3, 26–28, 95–96, 182–183, 593–604
 - differential gain, 87
 - differential input resistance parameter, 209
 - differential input voltage range, 219–220
 - differential integrator, 562–563
 - differential large signal voltage amplification parameter, 195–196
 - differential nonlinearity error, 328
 - differential phase error parameter, 227
 - digital circuitry, 495–496
 - digital ground, 484
 - dominant pole compensation, 105–108, 118
 - double integrator, 562
 - double pole filter, 158
 - DR (dynamic range), 507, 509–511
 - drift, minimizing, 88
 - DSP (digital signal processor), 274
 - dual supply amplifier, single supply vs., 35–37
 - dual supply amplifier packages, 500
- E**
- ENOB (effective number of bits), 331
 - equivalent input noise voltage parameter, 222
 - error, sources of, 87.
 - See also* application errors
 - error budget, 236, 321–326
 - error correction, 474
 - error terms, 511*t*
 - externally compensated amplifier, 88, 104
 - external V_{REF} circuits for ADCs/DACs, 287–290
- F**
- Fairchild, $\mu A709$, 4
 - fall time parameter, 213
 - Faraday cage, 499
 - feedback, negative, 1, 88
 - feedback capacitance, 134–135
 - feedback circuits
 - Bode analysis of, 74–80
 - electronic, defined, 69

feedback filter, 158–160
 feedback loop, 553–554
 canonical, 72, 72*f*
 feedback networks, complex,
 28–30
 feedback resistor selection,
 130–133
 feedback resistor shorted,
 542–544
 feedback system analysis
 block diagram math and
 manipulations, 68–72
 feedback equation and
 stability, 72–74
 graphical techniques, 74–80
 historically, 2
 second order equation and
 ringing/overshoot
 predictions, 83–85
 stability
 calculating historically, 2
 capacitance and, 134–135
 loop gain plots for
 understanding, 80–83
 feedback systems
 multiloop, reducing to single
 loop, 69
 canonical form, 72, 72*f*, 342
 design, historically, 2
 multiloop, 69
 negative, 342
 feedback theory, purpose of
 studying, 67
 filter, defined, 365. *See also*
 specific filter types
 filter circuit biasing, 419–422
 filter circuits, 156–161
 filter design for beginners,
 453–472. *See also specific*
 filter types
 flicker noise, 172–173
 Fliege notch filter, 463
 flux residue, 495
 forward transmission S_{21} ,
 305–306
 frequency condition, 200

FSV, 233
 full wave rectifier circuit, 585
 fully differential amplifier
 application mistakes, 544–546
 basics, 147–148
 filter circuits, 156–161
 gain stages, 149–150
 incorrect common mode range,
 548–549
 incorrect DC operating point,
 546–548
 incorrect single ended
 termination, 544–546
 instrumentation amplifier, 155
 introduction, 147
 second output of, 148–149
 single ended conversion,
 150–151
 terminated inputs calculator,
 online, 151–152
 V_{OCM} pin, 153–155

G

gain
 amplifier gain, 302
 sine wave oscillators, 345
 stages, 149–150
 gain compensation, 108–109, 118
 gain error, 327–328
 gain margin, 193–194
 gain parameters
 gain bandwidth product
 parameter, 200
 gain margin parameter,
 193–194
 large signal voltage
 amplification gain
 condition, 195
 open loop voltage gain,
 194–195
 George A. Philbrick Research, 3
 grounding consideration in PCB
 design, 480–484
 GSM receiver (global system for
 mobile communications),
 273

H

Hall effect sensors, 242
 harmonic distortion,
 324–325
 harmonic distortion parameters,
 213–215
 harmonics, intermodulation,
 310–311
 high gain control systems, 80
 high level output voltage
 condition or parameter,
 223
 high pass filter, 32, 374
 high pass filter design,
 388–395, 442–443,
 453–454
 high speed analog input drive
 circuits, 290–293
 high speed filter design
 bandpass filters, 454–463
 conclusions, 472
 high pass filters, 453–454
 introduction, 453
 low pass filter, 453
 notch filters, 463–472

I

IC op amp, 4, 498
 ideal feedback equation, 90
 ideal op amp
 assumptions, 21–22
 destruction of the universe
 and, 32–34
 diagram, 23*f*
 specifications, 32
 IF receiver, 271.
 See also wireless
 communication systems
 image plane effect, 479
 impedance, VFAs vs. CFAs,
 144–145
 inductors, 487, 493–494
 input bias current parameter,
 201–202
 input capacitance and stability,
 133

- input capacitance parameters, 197–198
 - common mode input, 198
 - differential, 198
 - input current range parameter, 201
 - input noise current parameter, 202–203
 - input offset current parameter, 202
 - input offset voltage long term drift parameter, 229
 - input offset voltage parameter, 220–221
 - input resistance parameter, 208–209
 - differential, 209
 - input voltage condition, 220
 - input voltage range condition or parameter, 218
 - instability effect, 2
 - instrumentation amplifier, 155, 551–552, 593
 - simplified, 552–553
 - intermodulation distortion, 332
 - intermodulation harmonics, 310–311
 - internally compensated amplifier, 88, 98–104, 118
 - interpolating filter, 285
 - inverted voltage reference circuit, 581
 - inverting amplifier, 24–25, 93–95
 - circuit analysis, 38–42
 - circuit noise model, 180–182
 - gain and offset matrix, 61
 - RF, 298
 - inverting attenuator
 - with negative offset, 64
 - with positive offset, 64
 - with zero offset, 63
 - inverting current feedback amplifier, 126–127
 - inverting differentiator, 564
 - with noise filter, 565–566
 - inverting integrator, 554–555
 - with drift compensation, 557
 - with electronic reset, 558–559
 - with input current compensation, 555–556
 - with mechanical reset, 557–558
 - with resistive reset, 559–560
- J**
- Johnson noise, 170, 175
- K**
- Kirchoff's voltage law, 8
- L**
- LC (inductance/capacitance) circuits, 341
 - lead compensation, 110–113, 118
 - lead/lag compensation, 116–117, 119
 - lead temperature for 10 or 60 seconds, 229
 - load capacitance condition, 198–199
 - load resistance condition, 209
 - lockup, 74, 91
 - loop antenna, 489
 - loop gain, 73, 80, 90, 108–109
 - loop gain plots, 80–83
 - low level output voltage
 - condition or parameter, 223
 - low pass filter design, 376–388
 - for beginners, 442
 - for high speed, 453
 - low pass filter optimizations
 - Bessel low pass filter, 372–373
 - Butterworth low pass filter, 371
 - Tschebyscheff low pass filter, 371–372
 - low pass filters, 31, 75, 365
 - fundamentals, 366–376
 - quality factor, 374
 - low voltage amplifier circuit design
 - DAC to actuator analog interface, 524–529
 - dynamic range, 509–511
 - input common mode range, 513–518
 - introduction, 507–509
 - output voltage swing, 518–519
 - shutdown and low current drain, 519–521
 - signal to noise ratio, 512–513
 - single supply, 521
 - transducer to ADC analog interface, 521–523
 - LRC filters, 365
 - LSB (least significant bit), 232
- M**
- magnetic fields, sensing, 242
 - measured variable, 231
 - MFB (multiple feedback bandpass) topology
 - bandpass filters, 400–401
 - high pass filters, 393–394
 - low pass filters, 384–385
 - modified Deliyannis vs., 458–459
 - Miller effect, 98
 - mixer circuit, 272
 - μ A709, 4
 - μ A741, 5
 - multiloop feedback systems, 69
 - multiple feedback filter, 158–160
- N**
- National Electrical Manufacturers Association (NEMA), 475
 - negative feedback, 1, 88
 - negative output, 148

noise. *See also specific types of*
 colors, 174–176
 DAC AC errors and
 parameters
 SINAD ratio, 330
 THD + N, 330
 defined, 165
 excess, 173
 isolation, 499
 op amp, 176–183
 rms vs. P-P, 163–165
 sources, 165, 474–475
 types of, 167–174
 units, 166–167
 noise corner frequency, 176–183
 noise energy, 163
 noise floor, 165
 noise parameters
 broadband noise, 222–223
 equivalent input noise voltage,
 222
 input noise current, 202–203
 total harmonic distortion plus
 noise (THD+N), 213–215
 noise reduction, 104
 noise theory
 application example, 183–188
 characterization, 163–167
 introduction, 163
 nonideal equations, development
 of, 87–96
 noninverting amplifier, 23–24,
 91–93
 circuit analysis, 41
 circuit noise model, 182
 gain and offset matrix, 61
 RF, 298
 noninverting attenuator
 with negative offset, 63
 with positive offset, 62
 with zero offset, 62
 noninverting current feedback
 amplifier, 124–125
 noninverting integrator
 approximation, 561–562
 with inverting buffer, 560–561

nonlinearity error, 329–330
 Norton's theorem, 12
 notch filter, 578–579
 notch filter design
 for beginners, 447–449
 for high speed, 463–472
 null resistance condition, 210

O

offset error, 326–327
 Ohm's law, 8
 1/f noise, 172
 op amp gain, 87
 op amps. *See also specific
 types of*
 compensated attenuator
 applied to, 113–115
 differential vs. single
 ended, 3
 error sources, 87
 functions of, 5
 historically, 21–22, 137
 operated at less than unity,
 533–535
 packages, 499–503
 parameters comparison,
 529–531
 self-destructive, 24
 single ended, 147
 stability, 4, 24
 summary, 531–532
 unused sections, 503,
 538–540
 open loop gain, 87
 open loop parameter
 transimpedance, 227
 transresistance, 210
 voltage gain, 194–195
 operating free air temperature
 condition, 212–213
 optical transducers, 240
 oscillation
 frequency, 344
 requirements for, 342–343
 oscillator design, 80, 342

oscillators. *See also specific
 types of*
 classes of, 341
 stable, 344
 oscillatory, 74, 91
 output current condition, low
 level, 203
 output current parameters, 203
 short circuit, 203
 output impedance parameter,
 225–226
 output resistance parameter, 210
 output voltage parameters
 high level, 223
 low level, 223
 output voltage swing parameters
 maximum peak to peak,
 223–224
 peak to peak, 225
 oversampling, 277
 overshoot/ringing predictions,
 83–85

P

parameters. *See data sheet
 parameters; specific
 parameters*
 PCB (printed circuit board)
 design
 basics, 473–475
 decoupling, 495–498
 error correction, 474
 example, 483
 grounding, 480–484
 input and output isolation, 499
 mechanical characteristics,
 475–480
 packages, 499–503
 passive component selection,
 484–495
 summary, 504–505
 peak follower circuit, 583
 peak to peak output voltage
 swing condition or
 parameter, 225

performance, external
 compensation and, 104
 phase linearity, RF design,
 307–308
 phase margin, 97
 phase margin parameter, 227
 phase shift oscillators
 buffered, 357–358, 571–572
 classical, 570–571
 sine wave, 343–345
 single amplifier, 356–357
 phototransistor, 240
 photovoltaic cell circuit, 241
 physics, laws of, 8–9
 pink noise, 175–176
 pole, 76
 pole compensation. *See* dominant
 pole compensation
 pole/zero combination, 76
 popcorn noise, 173, 176
 positive output, 148
 potentiometer, 237
 power booster, 339, 582–583
 power dissipation parameter,
 204
 power supply rejection ratio
 parameter, 204–205, 330
 power supply sensitivity, 330
 P-P vs. rms noise, 163–165
 precision rectifier circuit, 584

Q

quadrature oscillator, 360–361,
 569–570
 quad supply op amp packages,
 500

R

R/2R DAC, 318–320
 radiated noise, 474, 499
 radio noise, 278
 RC circuits, 341
 RC low pass filter, 366
 reactance, 31
 receiver noise, 278

reconstruction filter, 284–287
 red/brown noise, 176
 reference voltage
 characterization, 244–245
 reflections, 490–491
 relative stability, defined, 97
 relaxation oscillators, 341
 resistor ladder DAC, 316
 resistors, 485
 resolvers, 241
 resonators, 344
 return loss, 304–305
 reverse transmission S_{12} , 307
 RF amplifiers, 297–301
 RF conversion, 271.
 See also wireless
 communication systems
 RF design
 -1 db compression point,
 309–310
 advantages, 296
 amplifier gain, 302
 application error budget, 326
 conclusions, 314
 disadvantages, 296
 frequency response peaking,
 309
 introduction, 295
 noise figure, 312–313
 phase linearity, 307–308
 scattering parameters,
 302–307
 two tone, third order
 intermodulation intercept,
 310–311
 voltage vs. current feedback,
 296–297
 RF gain, 302
 RF stage performance, 302–307
 ringing/overshoot predictions,
 83–85
 rise time parameter, 216
 rms vs. P-P noise, 163–165
 RRI (rail to rail input), 515, 532
 RRIO op amp shutdown feature,
 532

RRO (rail to rail output), 518,
 532
 RTDs, 237

S

Sallen-Key topology
 bandpass filters, 398–400
 high pass filters, 391–394
 low pass filters, 380–384
 saturated transistor circuit, 17–18
 scattering parameters, RF design,
 302–307
 Schottky noise, 167.
 See also shot noise
 second order equation and
 ringing/overshoot
 predictions, 83–85
 semiconductor junctions, 242
 settling time parameter, 216–217,
 332–334
 short circuit current duration, 228
 short circuit output current
 parameter, 203
 shot noise, 165, 167–170, 175
 shutdown
 low current drain and,
 519–521, 532
 shutdown parameters
 turn off time, 213
 turn off voltage parameter, 220
 turn on time, 213
 turn on voltage, 220
 sigma delta DAC, 320–321
 signal chain design, 65
 signal source condition, 210
 simulated inductor, 576–578
 SINAD ratio, 330
 sine wave oscillators
 active element impact on,
 345–348
 analysis of the operation,
 348–349
 characterization, 341–342
 circuits, types of, 349–358
 gain in, 345

- phase shift in, 343–345
 - requirements for oscillation, 342–343
 - single amplifier phase shift oscillator, 356–357
 - single ended amplifier, 147–148, 150–151
 - single-ended termination, 544–546
 - single pole filters, 157
 - single supply amplifier
 - deficiencies, 40
 - dual supply vs., 35–37
 - single supply amplifier design
 - application mistakes, 544–546
 - circuit analysis, 38–42
 - DC offsets and, 339–340
 - gain and offset matrix, 61
 - incorrect single ended termination, 544–546
 - inverting attenuation, 63
 - noninverting attenuator, 62
 - recommended procedure, 42, 58
 - signal chain design, 65
 - simultaneous equation case forms, 42–58
 - summary, 58–59
 - single supply amplifier packages, 500
 - single supply circuits
 - absolute value, 583
 - AC integrator, 563
 - AC to DC converter, 585
 - attenuation circuit, 574–576
 - augmented differentiator, 566
 - augmenting integrator, 564
 - bandpass filter (BPF), 578–579
 - bubba oscillator, 572–573
 - buffered phase shift oscillator, 571–572
 - classical phase shift oscillator, 570–571
 - constant current generator, 580
 - curve fitting filters, 588–591
 - differential integrator, 562–563
 - double integrator, 562
 - full wave rectifier, 585
 - instrumentation amplifier, 551–552
 - simplified, 552–553
 - inverted voltage reference, 581
 - inverting differentiator, 564
 - with noise filter, 565–566
 - inverting integrator, 554–555
 - with drift compensation, 557
 - with electronic reset, 558–559
 - with input current compensation, 555–556
 - with mechanical reset, 557–558
 - with resistive reset, 559–560
 - noninverting integrator
 - approximation, 561–562
 - with inverting buffer, 560–561
 - notch filter, 578–579
 - peak follower, 583
 - power booster, 582–583
 - precision rectifier, 584
 - quadrature oscillator, 569–570
 - simulated inductor, 576–578
 - T network in the feedback loop, 553–554
 - tone control, 586–587
 - triangle oscillator, 573–574
 - twin T filter, 578–579
 - Wien bridge oscillator, 566–567
 - with AGC, 568–569
 - with nonlinear feedback, 567–568
 - sinusoidal oscillators, 341
 - slew rate parameter, 210–212
 - SNR (signal to noise ratio), 165, 512–513, 531
 - solar cell circuit, 241
 - spurious free dynamic range, 331–332
 - stability
 - compensation and, 88
 - current feedback op amp
 - analysis, 122–124, 127–130, 133, 134–135
 - defined, 97, 143
 - external compensation and, 104
 - feedback capacitance and, 134–135
 - feedback equation and, 72–74
 - feedback resistor selection for, 130–133
 - input capacitance and, 133
 - internal compensation and, 98
 - loop gain plots for understanding, 80–83
 - relative, 97
 - VFAs vs. CFAs, 143–144
 - step voltage peak to peak condition, 225
 - storage temperature parameter, 217
 - summing points, 69
 - superposition, 15–16
 - supply current parameter, 201
 - shutdown, 201
 - supply rejection ratio parameter, 204
 - supply voltage condition, 217–218
 - supply voltage sensitivity, 199
 - synchros, 241
- T**
- temperature parameters
 - case temperature for 60 seconds, 228
 - lead temperature for 10 or 60 seconds, 229
 - maximum junction temperature, 216

- temperature parameters
(*Continued*)
 - maximum junction temperature parameter, 216
 - operating free air temperature condition, 212–213
 - storage temperature, 217
- temperature transducers, 242, 245
- termination, improper, 538–540
- thermal noise, 165, 170–172, 175, 278
- thermal resistance parameter
 - junction to ambient, 205–207
 - junction to case, 207–208
- thermistors, 237
- thermocouples, 242
- Thevenin's theorem, 11–15
- through hole amplifier, 502–503
- TL07X, 100
- TLV277X, 102
- T network, 28
 - in the feedback loop, 553–554
- tone control circuit, 586–587
- traces in PCB design, 488–490
- trace to plane capacitors, 491–493
- trace to trace capacitors and inductors, 493–494
- transducer/ADC combinations, 231–236
- transducer measurement system
 - ADC characterization in, 247–248
 - amplifier circuit design, 249–256
 - design procedure, 243–244
 - introduction, 231–236
 - op amp selection in, 248
 - reference voltage
 - characterization, 244–245
 - summary, 257
 - system specifications review, 244
 - testing, 256
 - transducer characterization in, 245–247
 - transducer measurement system design specifications
 - guaranteed but not tested (GNT), 235
 - guaranteed by design (GBD), 235
 - guaranteed minimum/maximum, 235
 - typical, reasons to not use, 235
 - transducer resistance, 237
 - transducers. *See also specific types of*
 - ADC analog interface, 231–236
 - ADC interface, 521–523
 - characterization, 245–247, 512
 - error budget, 236
 - selection criteria, 231, 237
 - types of, 237–242
 - transistor amplifier, 18–20
 - transistor circuits, saturated, 17–18
 - transistor era, 4
 - transistors, options to, 295
 - triangle oscillator, 573–574
 - Tschebyscheff low pass filter, 371–372, 403*t*, 428–437
 - turn off time parameter, 213
 - turn off voltage parameter, 220
 - turn on time parameter, 213
 - turn on voltage parameter, 220
 - twin T filter, 409–410, 463, 578–579
 - two pole circuit, 83
 - two slope transfer function, 81
- U**
 - unity gain bandwidth parameter, 196
 - unity gain buffer, 24
 - unity gain stable, 533–535
 - unused sections, 503, 538–540
- V**
 - vacuum tube era, 3–4
 - VFA (voltage feedback amplifier), 97, 281, 341
 - CFAs vs., 121, 127, 152
 - via, 494–495
 - video amplifiers, 30, 121
 - V_{ocm} (voltage output common mode (level)), 153–155, 548–549
 - voltage amplification gain
 - condition, large signal, 195
 - voltage booster, 337–339
 - voltage divider circuit, 237
 - voltage divider rule, 9–10, 23
 - voltage feedback compensation
 - comparison of schemes, 118–119
 - compensated attenuator applied, 113–115
 - conclusions, 119
 - dominant pole, 105–108
 - external, stability, and performance, 104
 - gain, 108–109
 - internal, 98–104
 - introduction, 97–98
 - lead, 110–113
 - lead/lag, 116–117
 - voltage parameters
 - common mode input voltage condition, 218
 - common mode input voltage range, 218–219
 - differential input, 219
 - differential input voltage range, 219–220
 - differential large signal voltage amplification, 195–196
 - equivalent input noise voltage, 222
 - high level output voltage, 223
 - input offset voltage, 220–221

- input offset voltage long term drift, 229
 - input voltage condition, 220
 - input voltage range condition or parameter, 218
 - large signal voltage amplification gain condition, 195
 - low level output voltage, 223
 - open loop voltage gain, 194–195
 - output voltage swing
 - maximum peak to peak, 223–224
 - peak to peak, 225
 - step voltage peak to peak condition, 225
 - supply voltage condition, 217–218
 - supply voltage sensitivity, 199
 - turn off voltage (shutdown), 220
 - turn on voltage (shutdown), 220
 - voltage rails, 310
 - V_{REF} circuits (external) for ADCs/DACs, 287–290
 - VSWR (voltage standing wave ratio) S_{11} and S_{22} , 303
- W**
- W-CDMA transmit chain, 274
 - weighted resistor DAC, 317–318
 - Wheatstone bridge circuit, 237, 239
 - whip antenna, 488
 - white noise, 175
 - wideband amplifier, 281
 - Widler, Robert J., 4
 - Wien bridge oscillator, 350–356, 566–567
 - with AGC, 568–569
 - with nonlinear feedback, 567–568
 - Wien-Robinson filter, 411–412
 - wire junctions, 242
 - wireless communication systems
 - ADC/DAC-high speed op amp interface design
 - ADC/DAC selection, 276–281
 - antialiasing filters, 283–284
 - communication D/A converter reconstruction filter, 284–287
 - external V_{REF} circuits for ADCs/DACs, 287–290
 - high speed analog input drive circuits, 290–293
 - introduction, 271–276
 - op amp selection factors, 281–283
- Z**
- zero, 76